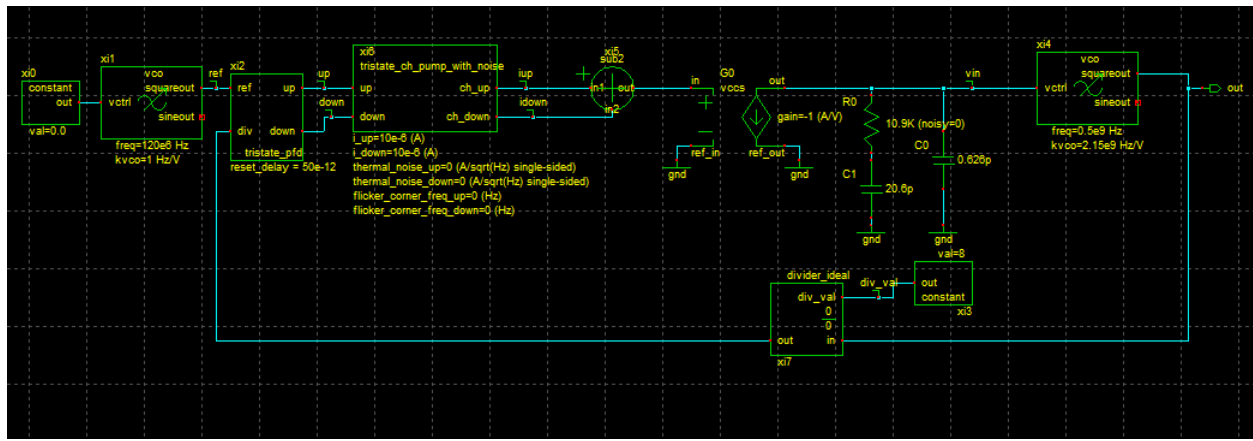


# Lab6

## Part 1

### 1-



### 2-

Result

215

Lower Limit

50

Upper Limit

400

Generate



Clear



$$KVCO = (215 / 100) * 1e9 = 2.15e9$$

$$3- f(out) = f(in) + Kvco * vin$$

$$8 * 120e6 = 0.5e9 + 2.15e9 * vin$$

$$Vin = 0.2139 V$$

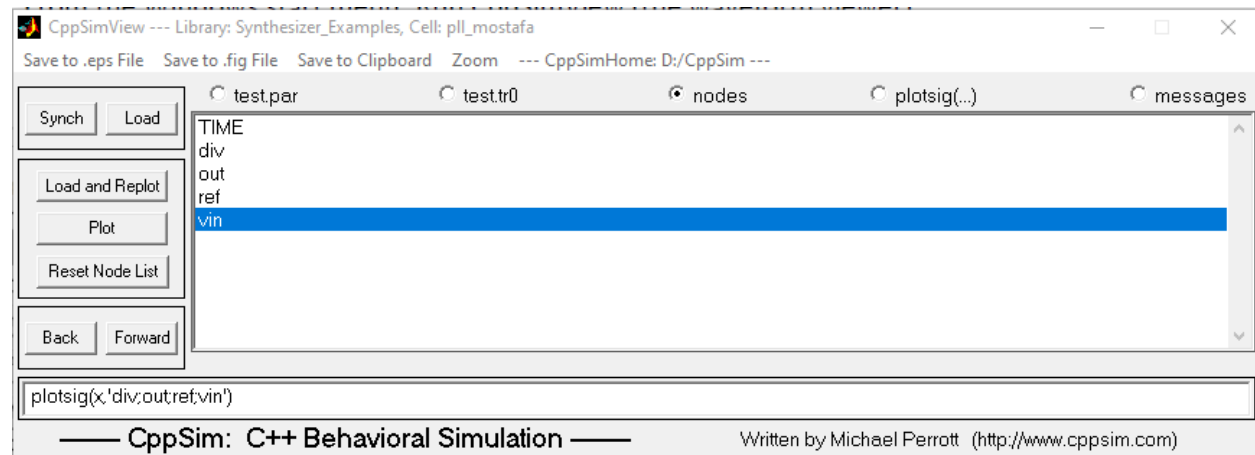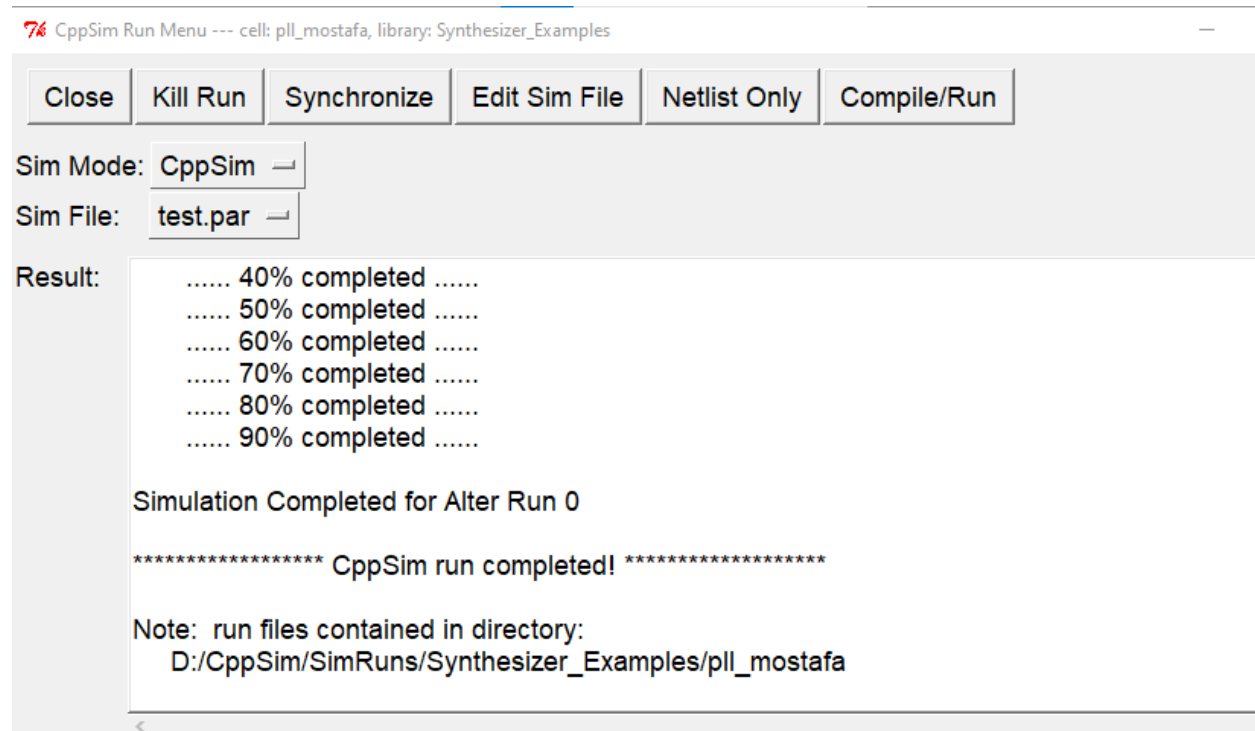


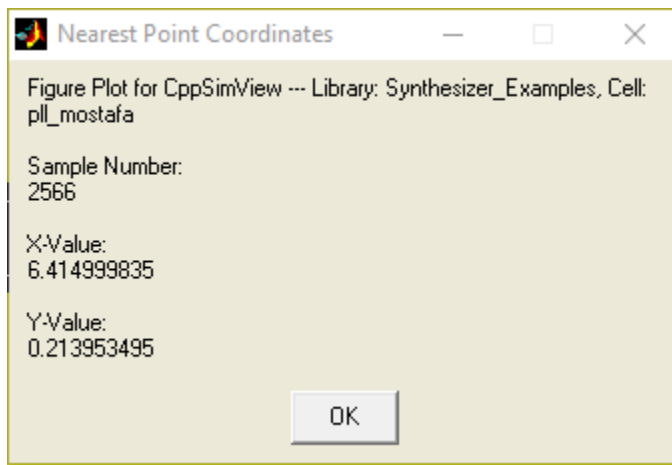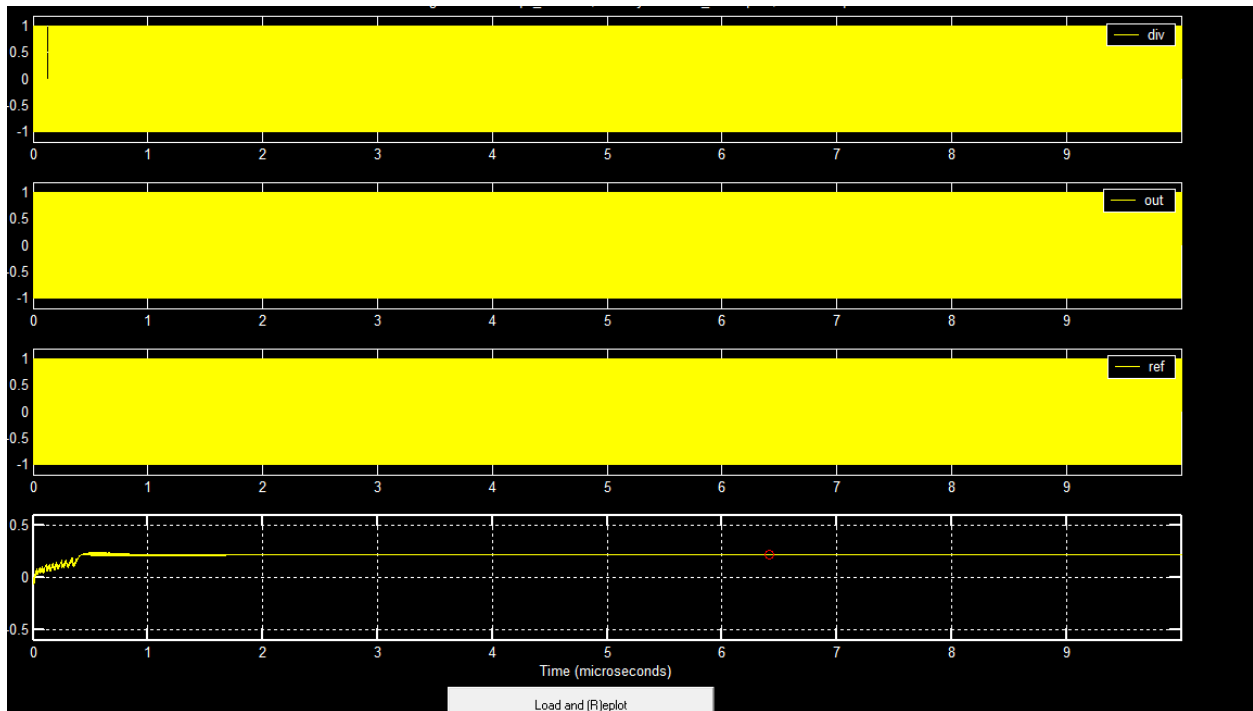


	Analytically	CppSim
Vin	0.2139	0.21395

We can observe that the value of  $V_{in}(V_{ctrl})$  from simulation is exactly the same as the value obtained analytically .

Before lock :


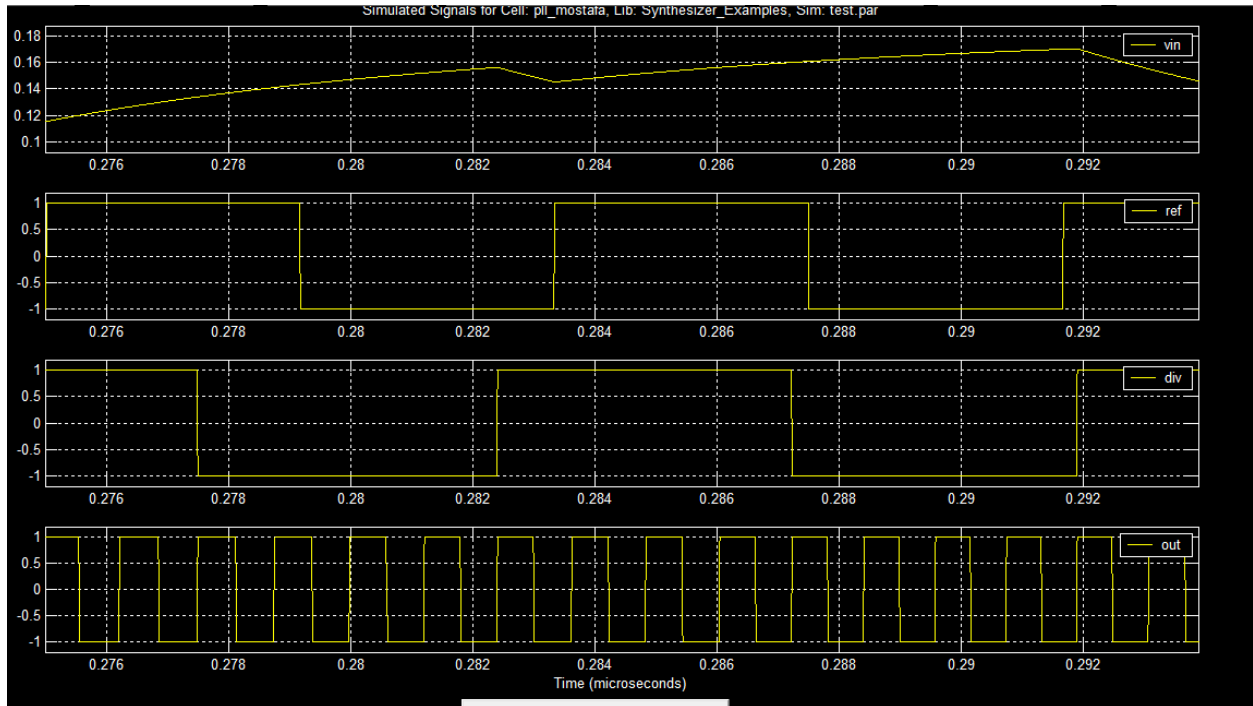


After lock:

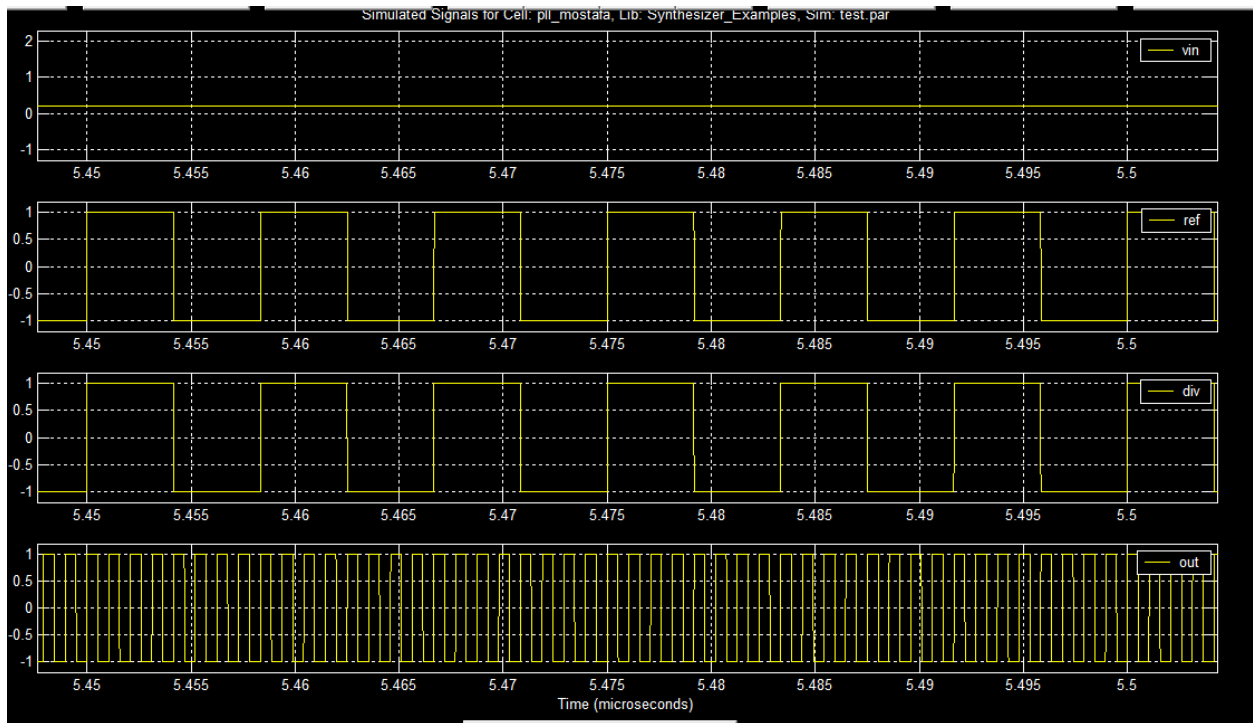


# Part 2


1-

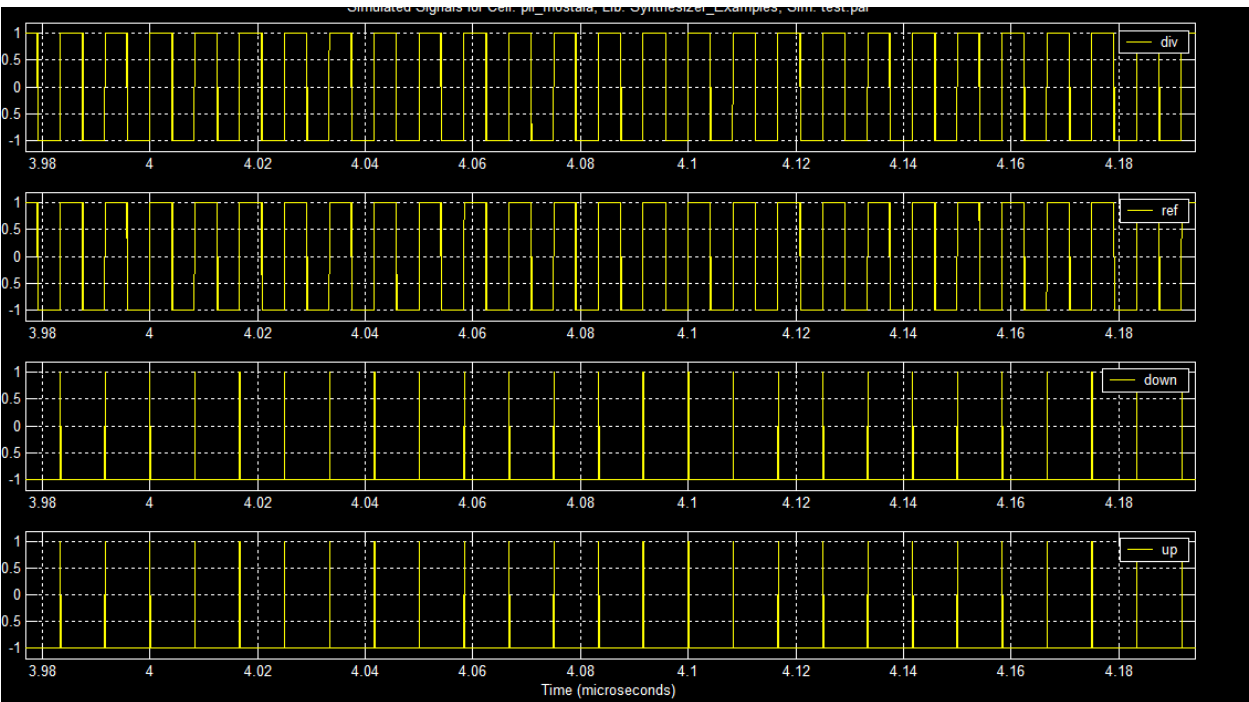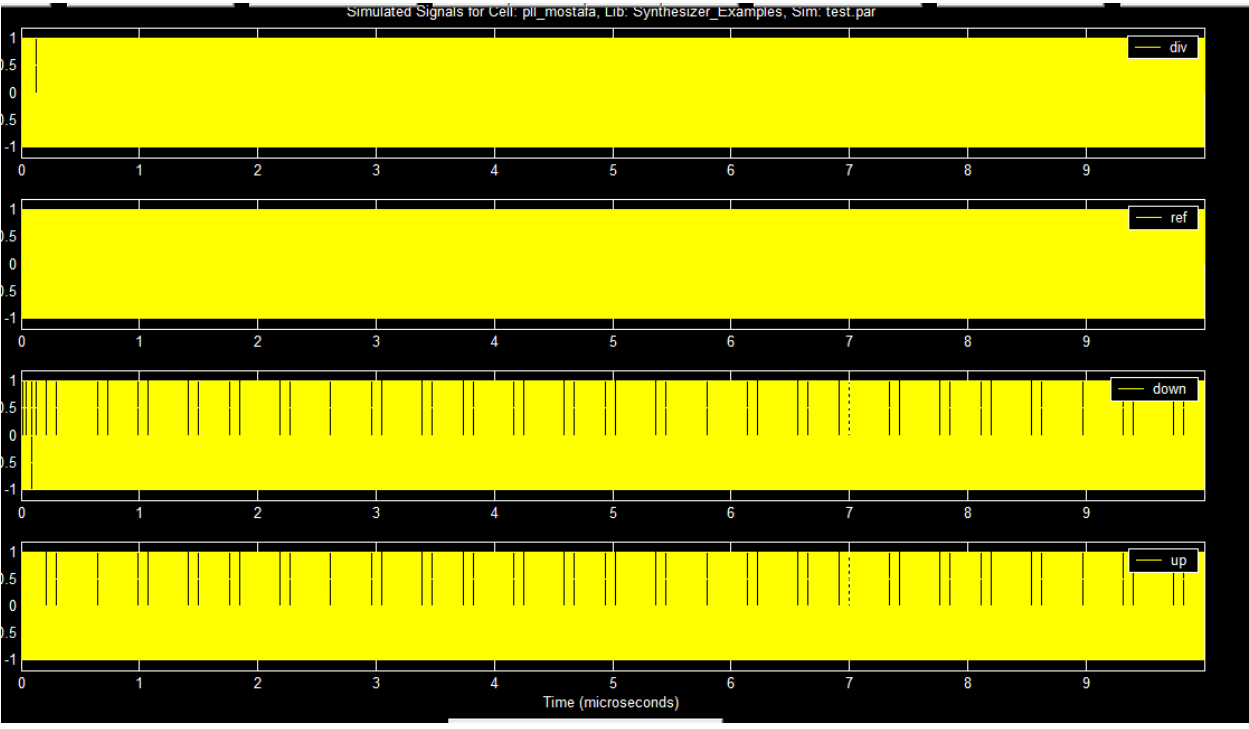


2-

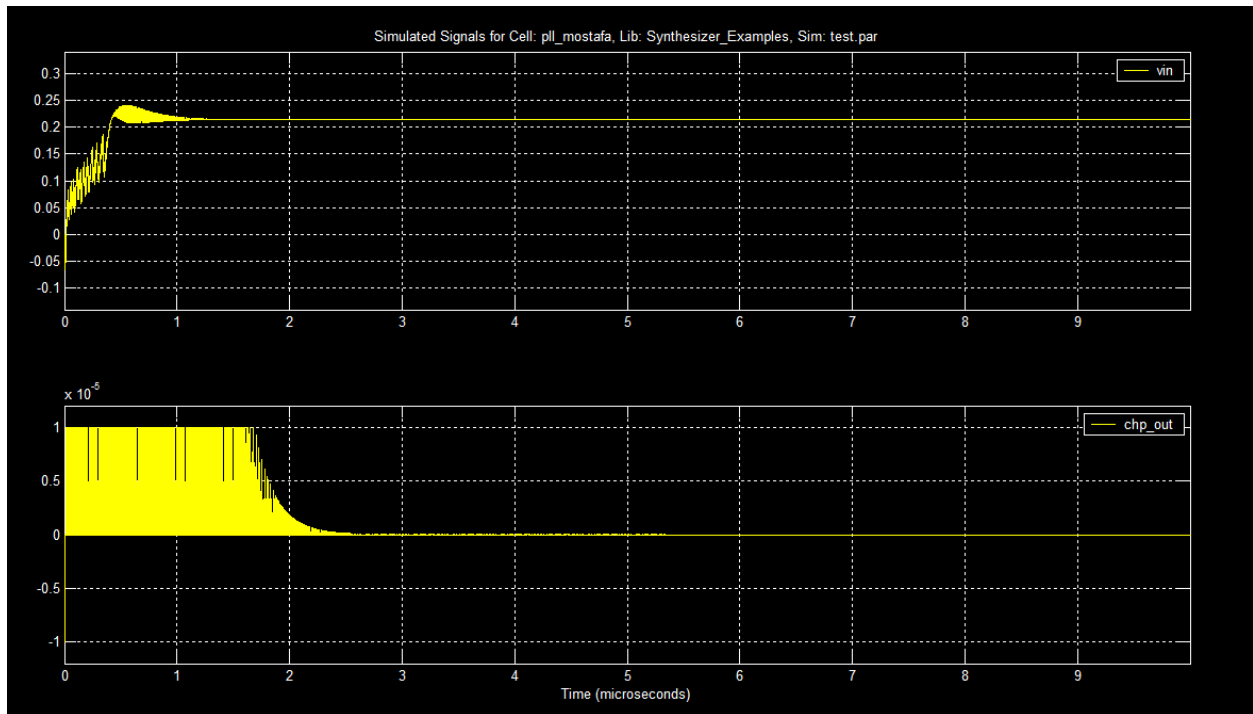



Before lock:

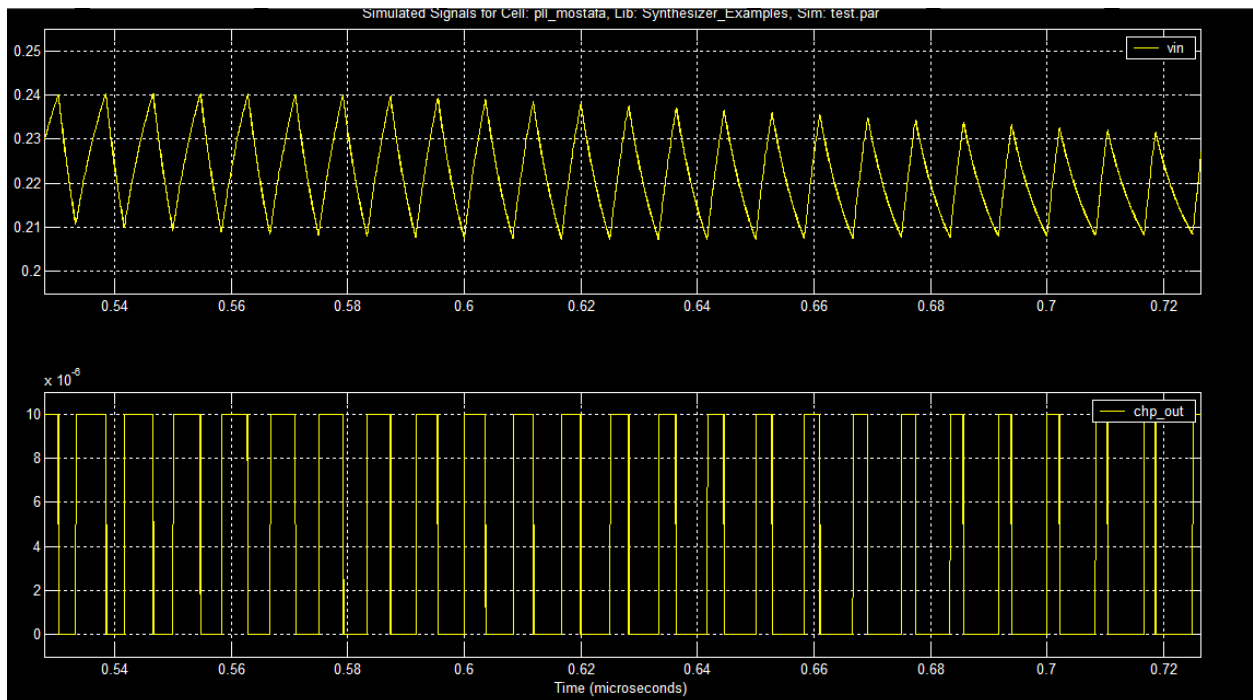


After lock:

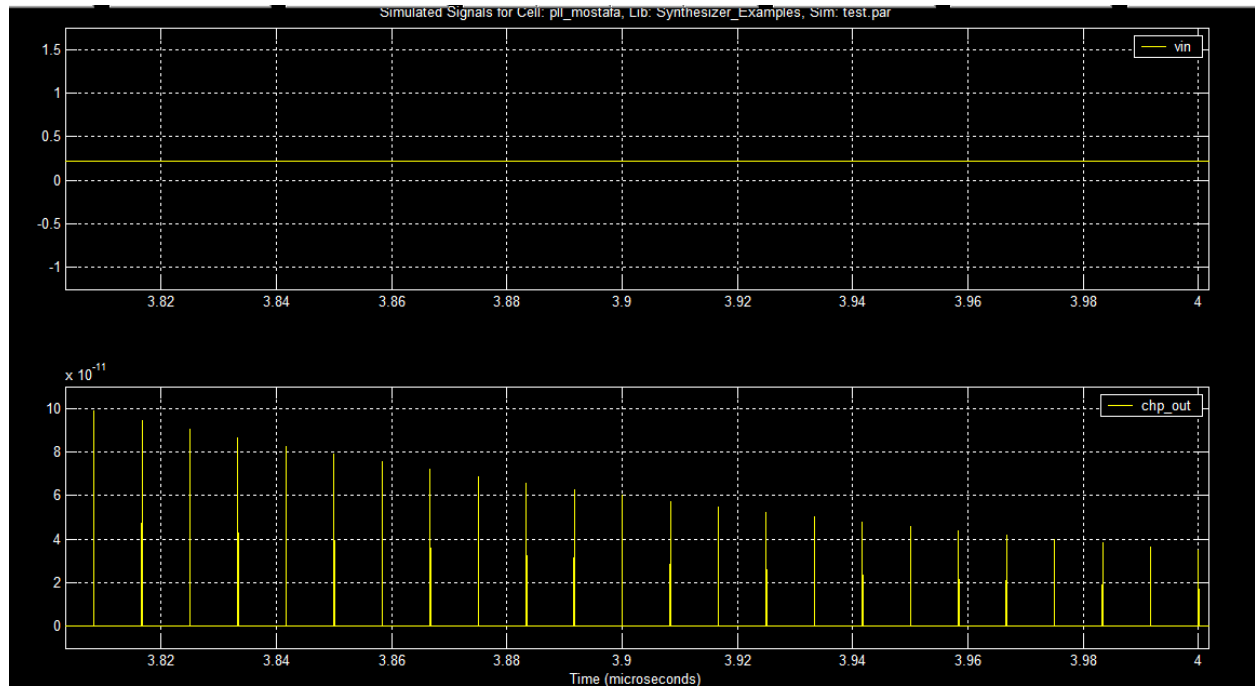

### Part 3

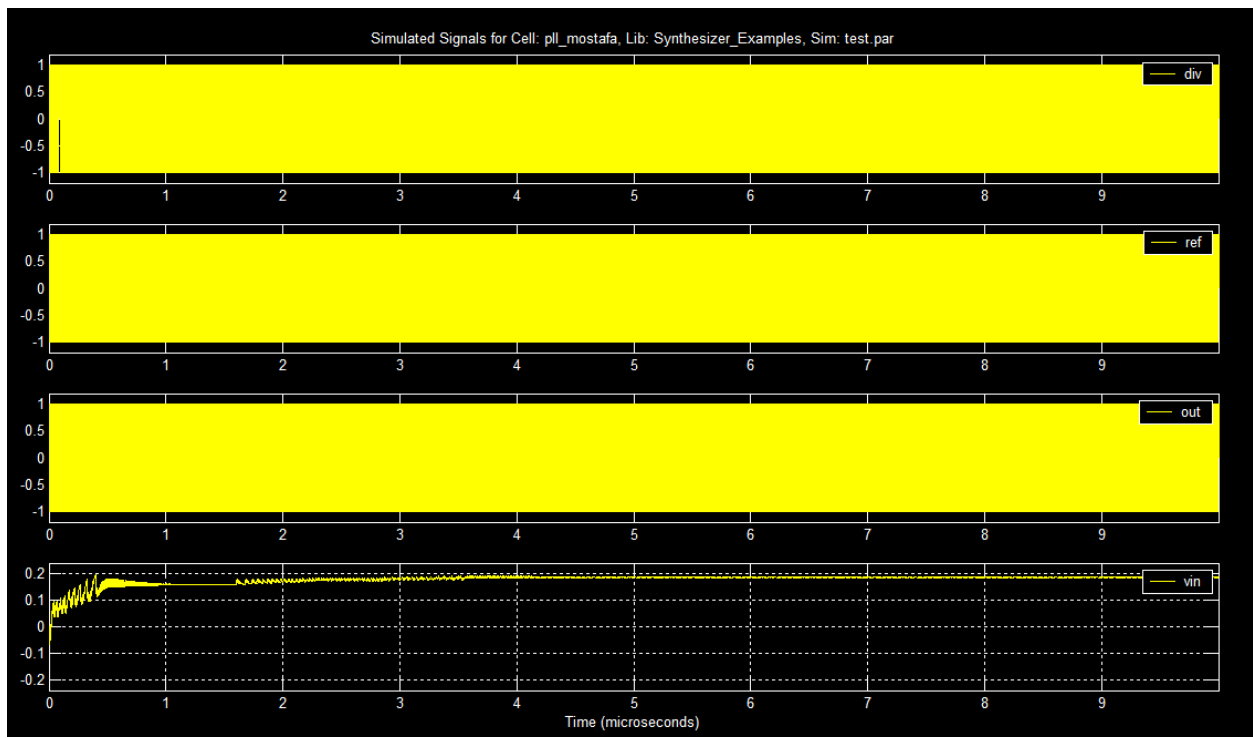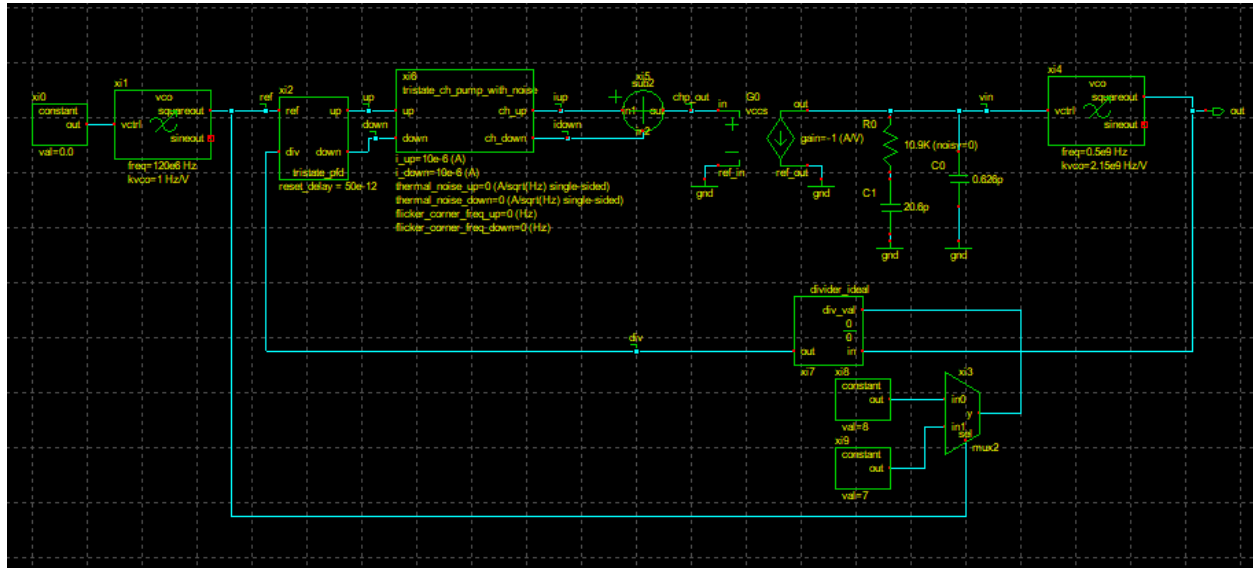



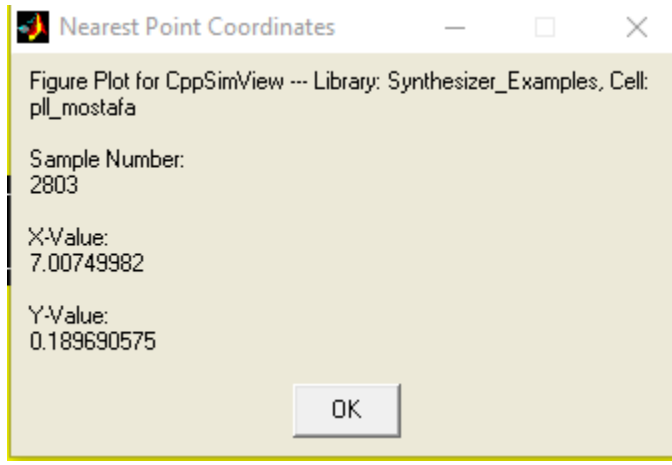

$$f(\text{out}) - f(\text{in}) = K_{vco} * v_{in}$$



$$7.5 * 120e6 = 0.5e9 + 2.15e9 * v_{in}$$

$$V_{in} = 0.186 \text{ V}$$


	Analytically	CppSim
Vin	0.186	0.18969

We can observe that the value of  $V_{in}(V_{ctrl})$  from simulation is near the value obtained analytically but not exactly the same because the  $V_{in}$  value isn't stable due to changing the divider value between 7 and 8 .

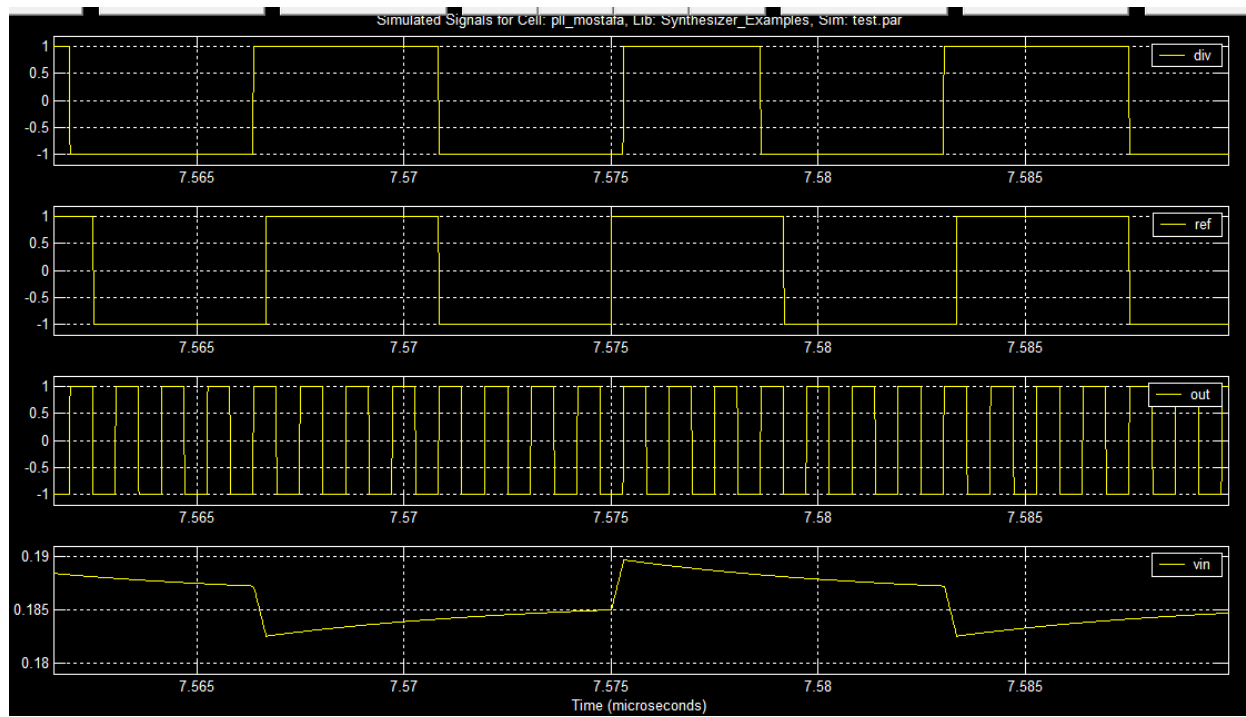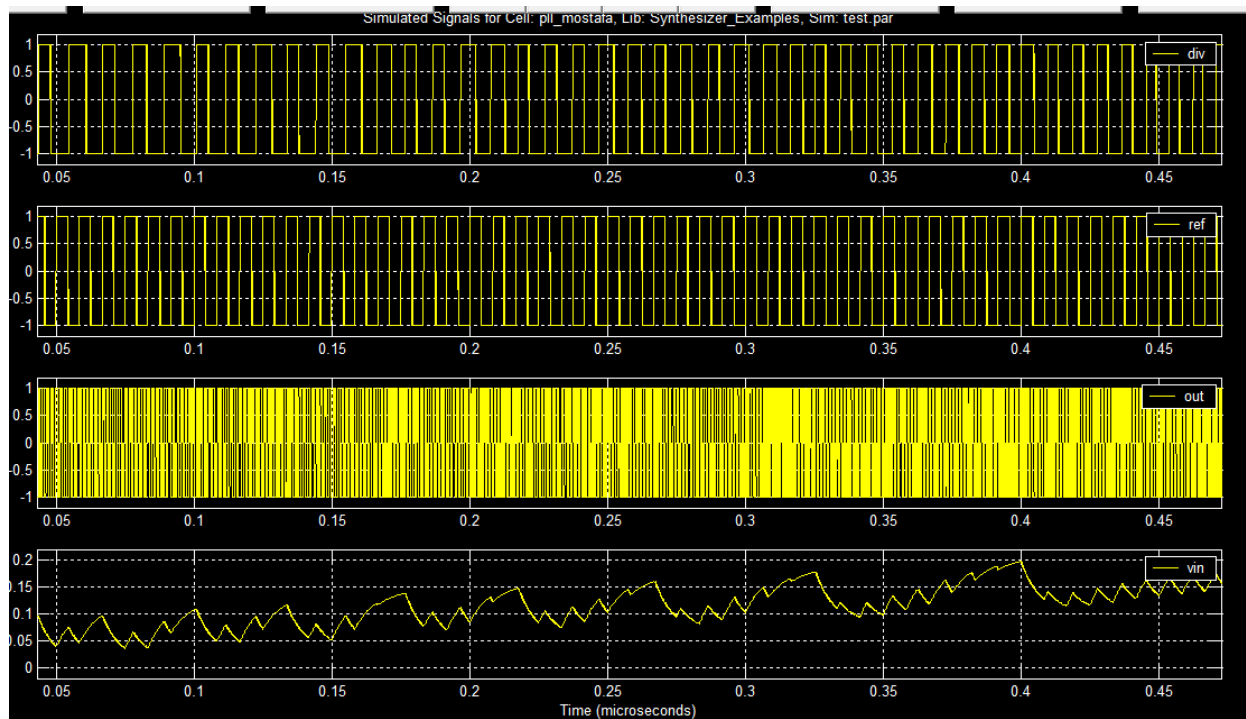Using mux to divide over two different values using the same divider made  $V_{in}$  not stable but gave us the effect of using fractional N divider so we substituted with  $N = 7.5$  in the equation .



3-

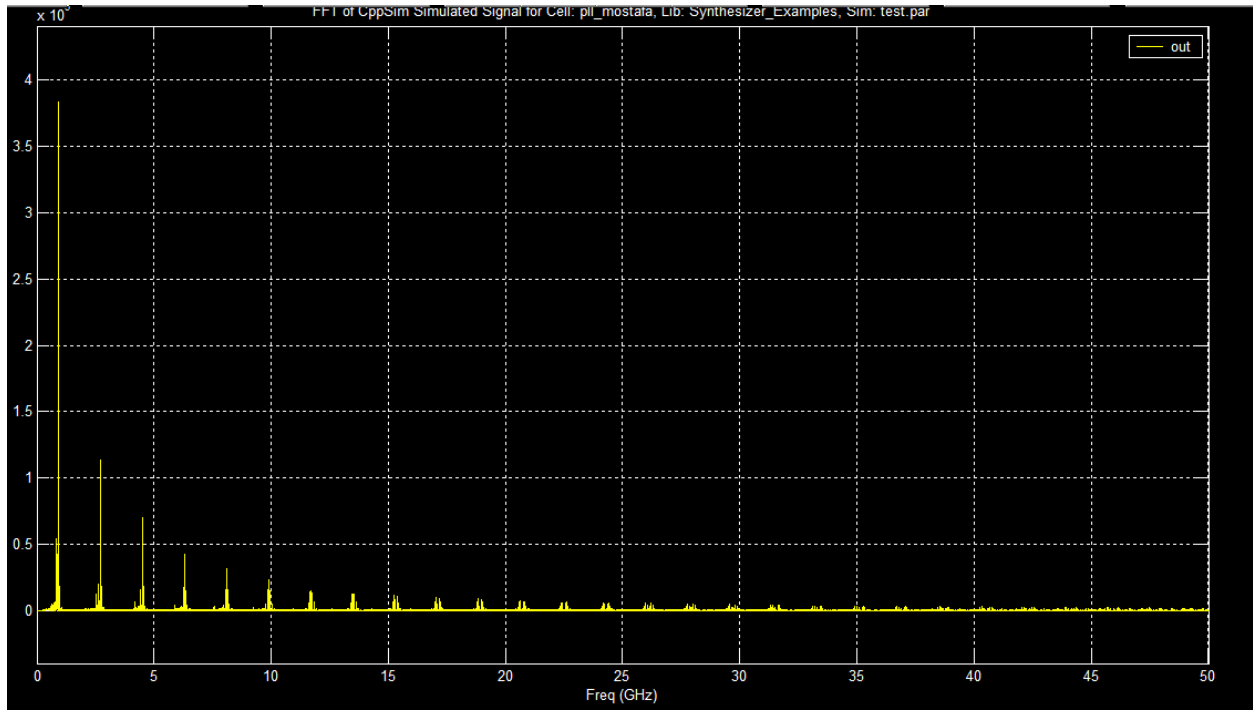

- 1- We can see the main tone at 0.96 GHz which aligns perfectly with the expected locked VCO frequency:

$$f_{vco} = N \cdot f_{ref} = 8 \cdot 120 \text{ MHz} = 960 \text{ MHz}$$

- 2- there is additional odd harmonics with decreasing power with high frequencies .

These are harmonics of the square-wave VCO output and because we are alternating between two divider values which introduces some unwanted spurs